

Class:		CPE200L - 1002		Semester:	Spring 2020
Points		Document author:	David Nakasone, Luis Cardenas		
		Author's email:	nakasd3@unlv.nevada.edu , Cardell1@unlv.nevada.edu		
		Document topic:	Post Lab 12 Final Project		
Instructor's comments:					

1. Description:

This a Group project of 2 people, David Nakasone & Luis Cardenas, in this project two devices are built one for encryption and the other for decryption. To realize these functions Verilog was used to code both the encryption and decryption devices. Two test benches are written respectively for the encryption and decryption device. The test bench stimulates this circuit by acting as the buffer for an arbitrary plain text input stream. Both devices Input 200 words of 16-bit length and then output 200 words of 16-bit length. If the message is less than 200 words, the NULL character will be encrypted. This project is comprised of 5 program files: one for getting the ascii message, a function for encryption, its respective testbench function, a decryption function, and its respective testbench.

2. Background and Theory:

This is a 2-circuit project; for this to work the sender and receiver (both parties) should each have an encryption or/and decryption circuit so they can both transmit and receive. The first circuit is an encryption device is designed to input 200 unencrypted 16-

bit words and then output 200 16-bit words; that encrypt the original input. In each word, the input represents a 7-bit ASCII character that the sender wants to transmit, starting with the LSB of the 16-bit word. The remaining bits are 0. The 16-bit word is encrypted on each rising clock edge. For encryption, the 16-bit word just adds $\{2^{15} + 1957\} = **34725**$ to the input, producing an output. In binary, the key is 16'b 1000 0111 1010 0101; for example, 'A' input = ASCII 65 (decimal), so input is [0000 0000 0100 0001]. The input is encrypted to (decimal) $34725 + 65 = 34790$, so the output is [1000 0111 1110 0110] the process continues until all 200 words have been encrypted. If the message is less than 200 words, the NULL character will be encrypted.

The test bench stimulates this circuit by acting as the buffer for an arbitrary plain text input stream. It is what the sender used to input his message. Using these 200 unencrypted 16-bit words as stimuli, the input is changed between clock edges. As the stimuli provide input to the DUT and output is recorded by the test bench, this represents the point at which the receiver gets the encrypted message. Since the transmission was encrypted, the received data will not be coherent unless the receiver has the proper KEY.

The second circuit is a decryption device; it is customizable to virtually anything, but both parties must use the same encrypt and decrypt method. It is designed to input 200 encrypted 16-bit words and output 200 decrypted 16-bit words, revealing the message from the sender. In each word, the received input represents a character. Since the encrypted input was an unencrypted ASCII character with a key of $\{2^{15} + 1957\} = **34725**$ added to it. For example, if you input [1000 0111 1110 0110] to be able to perform the decryption the device will subtract decimal 34725 or binary 16'b 1000 0111 1010 0101.

this produces the output of [0000 0000 0100 0001], revealing the character 'A'; this process continues until all the characters have been decrypted.

The test bench simulates this circuit with 200 encrypted 16-bit words that would have come from the sending circuit. As the stimuli produce output, the receiver can easily convert the binary ASCII numbers to characters and read the message. The encryption method is customizable to virtually anything, but both parties must use the same encrypt and decrypt method.

3. Schematics, Diagrams, and Photos:

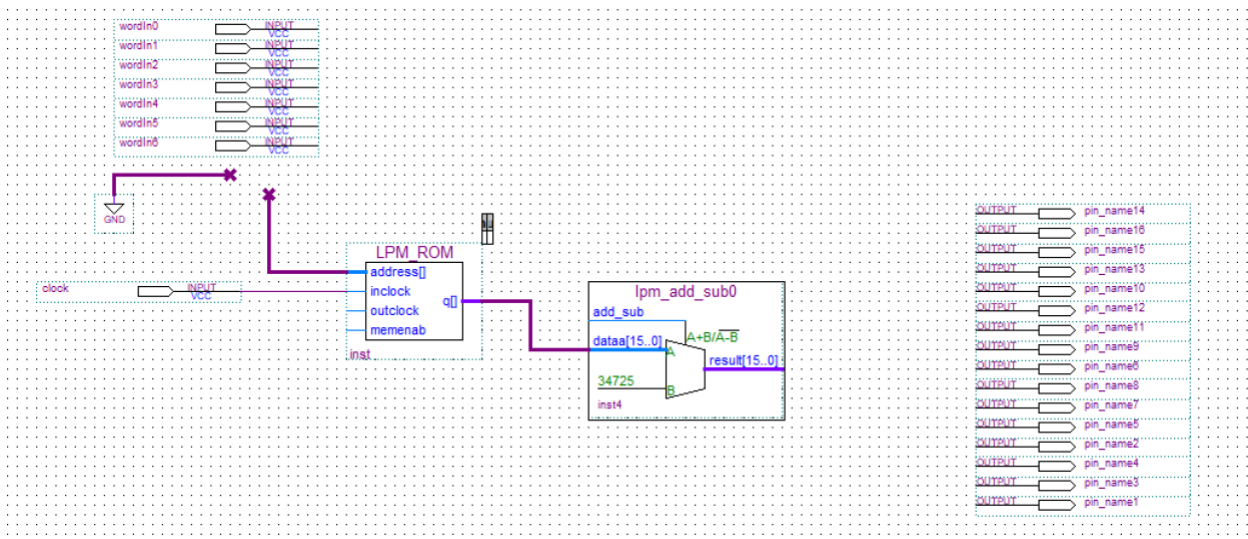


Fig (1) Encryption Device Code:

Quartus II 64-bit - C:/altera/13.0sp1/encryptor - encryptor

File Edit View Project Assignments Processing Tools Window Help

Project Navigator

Entity

Cyclone II: AUTO

encryptor

Tasks

low: Compila Customize...

13 reg [7:0] counter = 8'b0; // count to 199, reflects when all 200 lines encrypted, state control

14 //reg [15:0] carray = 16'b0; // takes input value to a register...for verification, but going to need more states

15 // reg [15:0] verify [0:199]; // holds the 200 lines of 16-bit input, can use to verify

16

17 always @ (posedge clock)

18 begin

19 if (abort)

20 begin

21 ps <= s0; // go to state 0 if abort = 1

22 wordOut <= 16'b0; // output is set to 0

23 readyTX <= 0; // not ready to TX

24 end

25 else ps <= ns; // otherwise go to next state

26 end

27

28

29 always @ (charIn, ps) // when present state or input changes

30 begin

31

32 case (ps)

33

34 s0: begin

35 wordOut = 16'b0; // output is 0

36 readyTX = 0;

37 ns = abort==0 ? s1 : s0; // if abort is 0, encryption can begin

38 end

39

40 s1: begin

41 wordOut = charIn + 16'b1000011110100101; // encrypt current character

42 counter = counter + 1; // increment counter

43 if (counter == 8'b11001000) ns = s2; // once 200 characters encrypted, proceed

44 else ns = s1; // keep encrypting if 200 characters have not been encrypted

45

46

47

1444

1

```

1 module encryptor (clock, abort, charIn, wordOut, readyTX); // end of
  port list
2
3   input clock;           // gets the 16-bit character every
  positive edge
4   input abort;           // cease and clear when = 1, synchronus
5   input [15:0] charIn;   // input as 16-bit ASCII character with
  only 7 bits used
6   output reg [15:0] wordOut; // output as 16-bit encrypted word
7   output reg readyTX;    // when circuit is ready to
  transmit, "readyT" = 1
8
9   parameter s0 = 0, s1 = 1, s2 = 2, s3 = 3; // states
10  reg [1:0] ps, ns;      // present state, next
  state registers
11  initial ps = 2'b00;    // start in state 0
12
13  reg [7:0] counter = 8'b0; // count to 199,
  reflects when all 200 lines encrypted, state control
14  //reg [15:0] carray = 16'b0; // takes input value to a
  register...for verification, but going to need more states
15  // reg [15:0] verify [0:199]; // holds the 200 lines of 16-
  bit input, can use to verify
16
17  always @ (posedge clock)
18  begin
19      if (abort)
20      begin
21          ps <= s0; // go to state 0 if abort = 1
22          wordOut <= 16'b0; // output is set to 0
23          readyTX <= 0; // not ready to TX
24      end
25      else ps <= ns; // otherwise go to next state
26  end
27
28

```

```

28
29 always @ (charIn, ps) // when present state or input changes
30 begin
31
32     case (ps)
33
34         s0: begin
35             wordOut = 16'b0; // output is 0
36             readyTX = 0;
37             ns = abort==0 ? s1 : s0; // if abort is 0,
encryption can begin
38             end
39
40         s1: begin
41             wordOut = charIn + 16'b1000011110100101;
42             // encrypt current character
43             counter = counter + 1; //
increment counter
44             if (counter == 8'b11001000) ns = s2; //
once 200 characters encrypted, proceed
45             else ns = s1; //
keep encrypting if 200 characters have not been encrypted
46             readyTX = 0;
47             end
48
49         s2: begin
50             readyTX = 1'b1; // ready to transmit encrypted
message
51             #100; // use counter or wait time to
reflect all bits leaving as serial TX
52             // good spot for a confirmation
53             ns = s3; // go to the "done state"
54             end
55
56         s3: begin
57             readyTX = 1'h1;
58             readyTX = 1'b1; // clear transmit buffer
59             wordOut = 16'b0; // clear input buffer
60             //charIn = 16'b0; // stand by for next
61             ns = s0;
62             end
63     endcase
64 end
endmodule

```

Fig (2) Encryption Testbench:

```
1 //`timescale 1ns / 100ps // unit in ns....#1 is a 1ns delay 10% error
  not synthesizable
2
3 module TBencrypt;
4     reg clock;           // toggled for clock pulse
5     reg abort;           // starts in 1, 0 to encrpyt, made = 1 to
  clear and abort
6     reg [15:0] charIn;   // the 16-bit representation of the input
  character, see input buffer
7     wire [15:0] wordOut; // the 16-bit representation of the encrypted
  input character, output
8     wire readyTX;        // after 200 characters encrypted and placed
  in buffer, this starts serial TX
9
10    integer counter;
11
12    encryptor DUT (clock, abort, charIn, wordOut, readyTX);
13
14    always #10 clock = ~clock; // set clock
15
16    initial              // initial block, holds serial input of characters
17    begin
18        clock = 1'b0; // start it at 0
19        abort = 1'b0; // proceed to encrypt
20        counter = 3'd0; // just for display contol
21        $display ("          TIME(ns)          index
  value(encrypted)");
22        #5 charIn = 16'b0000000000000000; // stops Mealy lag...starts
  the offset, but THROW AWAY, not part of TX
23
24        // BEGIN INPUT BUFFER (original message entered by sender)
25        #20 charIn = 16'b00000000001001001; counter = counter + 3'd001; //
  input 1
26        #20 charIn = 16'b00000000000100000; counter = counter + 3'd001; //
  input 2
27        #20 charIn = 16'b00000000001101000; counter = counter + 3'd001; //
```

```

input 200
225 // END INPUT BUFFER (original message entered by sender)
226
227
228 #20 counter = counter + 3'd001;
229 #20 counter = counter + 3'd001; abort = 1; // disables circuit,
ready to get another transmission
230
231 #100 $finish;
232 end
233
234
235
236 // BEGIN OUTPUT BUFFER (original message entered by sender, each
charater encrypted)
237
238 always @ (posedge clock) // always block reflects serial
transmission of encrypted inputs
239 begin
240 // $write ("%s" , wordOut); // was used to test, use if needed
241 if( counter > 0 && counter <= 200)
242 begin
243 $write ("%d ", $time);
244 $write ("%d", counter);
245 $display (" %b", wordOut);
246 end
247 else if (counter == 200) $display("transmission complete");
248 else if (counter == 201) $display (" { reset,
ready for next TX }");
249 else $display ("tranmission to follow:");
250 end
251
252 // END OUTPUT BUFFER (original message entered by sender, each
charater encrypted)
253
254 endmodule

```


Fig (3) Decryption Device Code:

```
1 module decryptor (clock, abort, wordIn, charOut, readyRX, SV/Verilog/Design
   port list
2
3   input clock;                // gets the 16-bit encrypted word
   every positive edge
4   input abort;                // cease and clear when = 1,
   synchronus
5   input [15:0] wordIn;        // input as 16-bit encrypted word
6   output reg [15:0] charOut;   // output as 16-bit ASCII character
   with only 7 bits used
7   output reg readyRX;         // when circuit is ready to
   transmit, "readyT" = 1
8
9   parameter s0 = 0, s1 = 1, s2 = 2, s3 = 3; // states
10  reg [1:0] ps, ns;           // present state, next
   state registers
11  initial ps = 2'b00;         // start in state 0
12
13  reg [7:0] counter = 8'b0;    // count to 199,
   reflects when all 200 lines encrypted, state control
14  //reg [15:0] carray = 16'b0; // takes input value to a
   register...for verification, but going to need more states
15  // reg [15:0] verify [0:199]; // holds the 200 lines of 16-
   bit input, can use to verify
16
17
18  always @ (posedge clock)
19  begin
20    if (abort)
21    begin
22      ps <= s0;                // go to state 0 if abort = 1
23      charOut <= 16'b0;        // output is set to 0
24      readyRX <= 0;            // not ready to RX
25    end
26  else ps <= ns;               // otherwise go to next state
27  end
```

```

29  always @ (wordIn, ps)      // when present state or input changes
30      begin
31
32          case (ps)
33
34              s0: begin
35                  charOut = 16'b0;          // output is 0
36                  readyRX = 0;
37                  ns = abort==0 ? s1 : s0;  // if abort is 0,
decryption can begin
38                  end
39
40              s1: begin
41                  charOut = wordIn - 16'b1000011110100101;  //
decrypt current word
42                  counter = counter + 1;                    //
increment counter
43                  if (counter == 8'b11001000) ns = s2;      //
once 200 characters encrypted, proceed
44                  else ns = s1;                             //
keep decrypting if 200 characters have not been decrypted
45                  readyRX = 0;
46                  end
47
48              s2: begin
49                  readyRX = 1'b1;  // ready to receive more, last
message decrypted
50                  #100;           // use counter or wait time to
reflect all bits in as serial RX
51                                 // good spot for a confirmation
signal
52                  ns = s3;        // go to the "done state"
53                  end
54
55              s3: begin
56                  readyRX = 1'b1;
57                  charOut = 16'b0; // clear receive buffer
58                  //charIn = 16'b0; // clear output buffer
59                  ns = s0;        // stand by to decrypt next RX
60                  end
61          endcase
62      end
63
64  endmodule
65

```

Fig (4) Decryption Testbench:

```
1 module TBdecrypt;
2
3     reg clock;           // toggled for clock pulse
4     reg abort;           // starts in 1, 0 to encrypt, made = 1 to
clear and abort
5     reg [15:0] wordIn;   // the 16-bit representation of the input
character, see input buffer
6     wire [15:0] charOut; // the 16-bit representation of the encrypted
input character, output
7     wire readyRX;        // after 200 characters encrypted and placed
in buffer, this starts serial TX
8
9     integer index;
10    integer counter;
11    reg [15:0] holder [0:199]; // creates that table you want for
memory
12
13
14    decryptor DUT (clock, abort, wordIn, charOut, readyRX);
15
16    always #10 clock = ~clock; // set clock
17
18    initial           // initial block, holds serial RX input of 16-bit
encrypted words
19    begin
20        $display("\n");
21        clock = 1'b0; // start it at 0
22        abort = 1'b0; // proceed to decrypt
23        counter = 3'd0; // just for display control
24        //$display ("          TIME(ns)      index
value(encrypted)");
25        #5 wordIn = 16'b0000000000000000; // stops Mealy lag...starts
the offset, but THROW AWAY, not part of RX
26
```

```

27
28 // BEGIN INPUT BUFFER (encrypted RX from sender)
29 #20 wordIn = 16'b1000011111101110; counter = counter + 3'd001; //
   encrypted input 1
30 #20 wordIn = 16'b1000011111000101; counter = counter + 3'd001; //
   encrypted input 2
31 #20 wordIn = 16'b1000100000001101; counter = counter + 3'd001; //
   encrypted input 3
32 #20 wordIn = 16'b100010000000110; counter = counter + 3'd001; //
   encrypted input 4
33 #20 wordIn = 16'b1000100000011011; counter = counter + 3'd001; //
   encrypted input 5
34 #20 wordIn = 16'b1000100000001010; counter = counter + 3'd001; //
   encrypted input 6
35 #20 wordIn = 16'b1000011111000101; counter = counter + 3'd001; //
   encrypted input 7
36 #20 wordIn = 16'b1000011111011000; counter = counter + 3'd001; //
   encrypted input 8
37 #20 wordIn = 16'b1000011111000101; counter = counter + 3'd001; //
   encrypted input 9
38 #20 wordIn = 16'b1000100000011001; counter = counter + 3'd001; //
   encrypted input 10
39 #20 wordIn = 16'b1000100000010100; counter = counter + 3'd001; //
   encrypted input 11
40 #20 wordIn = 16'b1000100000010011; counter = counter + 3'd001; //
   encrypted input 12
41 #20 wordIn = 16'b1000100000011000; counter = counter + 3'd001; //
   encrypted input 13
42 #20 wordIn = 16'b1000011111000101; counter = counter + 3'd001; //
   encrypted input 14
43 #20 wordIn = 16'b1000100000010100; counter = counter + 3'd001; //
   encrypted input 15

```

```

212 #20 wordIn = 16'b1000100000010011; counter = counter + 3'd001; //
    encrypted input 184
213 #20 wordIn = 16'b1000100000001010; counter = counter + 3'd001; //
    encrypted input 185
214 #20 wordIn = 16'b1000011111010011; counter = counter + 3'd001; //
    encrypted input 186
215 #20 wordIn = 16'b1000011110101111; counter = counter + 3'd001; //
    encrypted input 187
216 #20 wordIn = 16'b1000011111101100; counter = counter + 3'd001; //
    encrypted input 188
217 #20 wordIn = 16'b1000011111110100; counter = counter + 3'd001; //
    encrypted input 189
218 #20 wordIn = 16'b1000011111110100; counter = counter + 3'd001; //
    encrypted input 190
219 #20 wordIn = 16'b1000011111101001; counter = counter + 3'd001; //
    encrypted input 191
220 #20 wordIn = 16'b1000011111000101; counter = counter + 3'd001; //
    encrypted input 192
221 #20 wordIn = 16'b1000011111110001; counter = counter + 3'd001; //
    encrypted input 193
222 #20 wordIn = 16'b1000011111111010; counter = counter + 3'd001; //
    encrypted input 194
223 #20 wordIn = 16'b1000011111101000; counter = counter + 3'd001; //
    encrypted input 195
224 #20 wordIn = 16'b1000011111110000; counter = counter + 3'd001; //
    encrypted input 196
225 #20 wordIn = 16'b1000011110100101; counter = counter + 3'd001; //
    encrypted input 197
226 #20 wordIn = 16'b1000011110100101; counter = counter + 3'd001; //
    encrypted input 198
227 #20 wordIn = 16'b1000011110100101; counter = counter + 3'd001; //
    encrypted input 199
228 #20 wordIn = 16'b1000011110100101; counter = counter + 3'd001; //
    encrypted input 200
229 // END INPUT BUFFER (encrypted RX from sender)

```

```

232
233     #20 counter = counter + 3'd001;
234     #20 counter = counter + 3'd001; abort = 1; // disables circuit,
ready to get another transmission
235
236     $display("\n");
237     for (index = 1; index < 200; index = index + 1)
238         begin
239             $write ("%s" , holder[index]);
240         end
241     $display("\n");
242
243
244     #100 $finish;
245     end
246
247
248     // BEGIN OUTPUT BUFFER (decrypted RX displayed as ASCII)
249
250     always @ (posedge clock) // always block reflects serial decrypted
RX of encrypted inputs provided
251     begin
252
253         if( counter > 0 && counter <= 200)
254             begin
255                 //$write ("%d ", $time);
256                 //$write ("%d", counter);
257                 //$display (" %b", wordOut);
258                 $write ("%s",charOut);
259             end
260         else if (counter == 200) $display("decryption complete");
261         else if (counter == 201)
262             begin
263                 $write ("\n");
264                 $display ("                                { reset. ready to decrypt next
265                 $display("\n");
266                 $display("SECOND TRANSMISSION, MAKE SURE IT SAME AS FIRST
:");
267             end
268         else $display ("message to follow:");
269
270     end
271
272     // END OUTPUT BUFFER (decrypted RX displayed as ASCII)
273
274
275     always @ (posedge clock)
276     begin
277         if (counter >= 2 || counter <= 201)
278             begin
279                 //$write ("%s" , char);
280                 holder[counter] = charOut;
281                 //counter = counter + 1;
282             end
283     end

```

Fig (5) encryption input (raw):

TIME(ns)	index	value(encrypted)
tranmission to follow:		
30	1	1000011111101110
50	2	10000111111000101
70	3	1000100000001101
90	4	1000100000000110
110	5	1000100000011011
130	6	1000100000001010
150	7	10000111111000101
170	8	10000111111011000
190	9	10000111111000101

Fig (6) encryption output(encrypted):

3850	192	10000111111000101
3870	193	1000011111110001
3890	194	1000011111111010
3910	195	1000011111101000
3930	196	1000011111110000
3950	197	1000011110100101
3970	198	1000011110100101
3990	199	1000011110100101
4010	200	1000011110100101
{ reset, ready for next TX }		
tranmission to follow:		

Fig(7) decryption input is same as encryption output:

3850	192	1000011111000101
3870	193	1000011111110001
3890	194	1000011111111010
3910	195	1000011111101000
3930	196	1000011111110000
3950	197	1000011110100101
3970	198	1000011110100101
3990	199	1000011110100101
4010	200	1000011110100101
{ reset, ready for next TX }		
tranmission to follow:		

Fig (8) decrytpor output with verification

```
message to follow:
I have 3 tons of gold that I need you to pick up.
Be at Melli Bank 35.686 51.393 no later than 202005271300Z.
Bring an airplane, some tools, and 5lbs of potatoes.
Pay Dr. Greg when done.
GOOD LUCK
{ reset, ready to decrypt next RX }
```

SECOND TRANSMISSION, MAKE SURE IT SAME AS FIRST :

```
I have 3 tons of gold that I need you to pick up.
Be at Melli Bank 35.686 51.393 no later than 202005271300Z.
Bring an airplane, some tools, and 5lbs of potatoes.
Pay Dr. Greg when done.
GOOD LUCK
```

message to follow:

Fig(9) SM Chart Decryption Device:

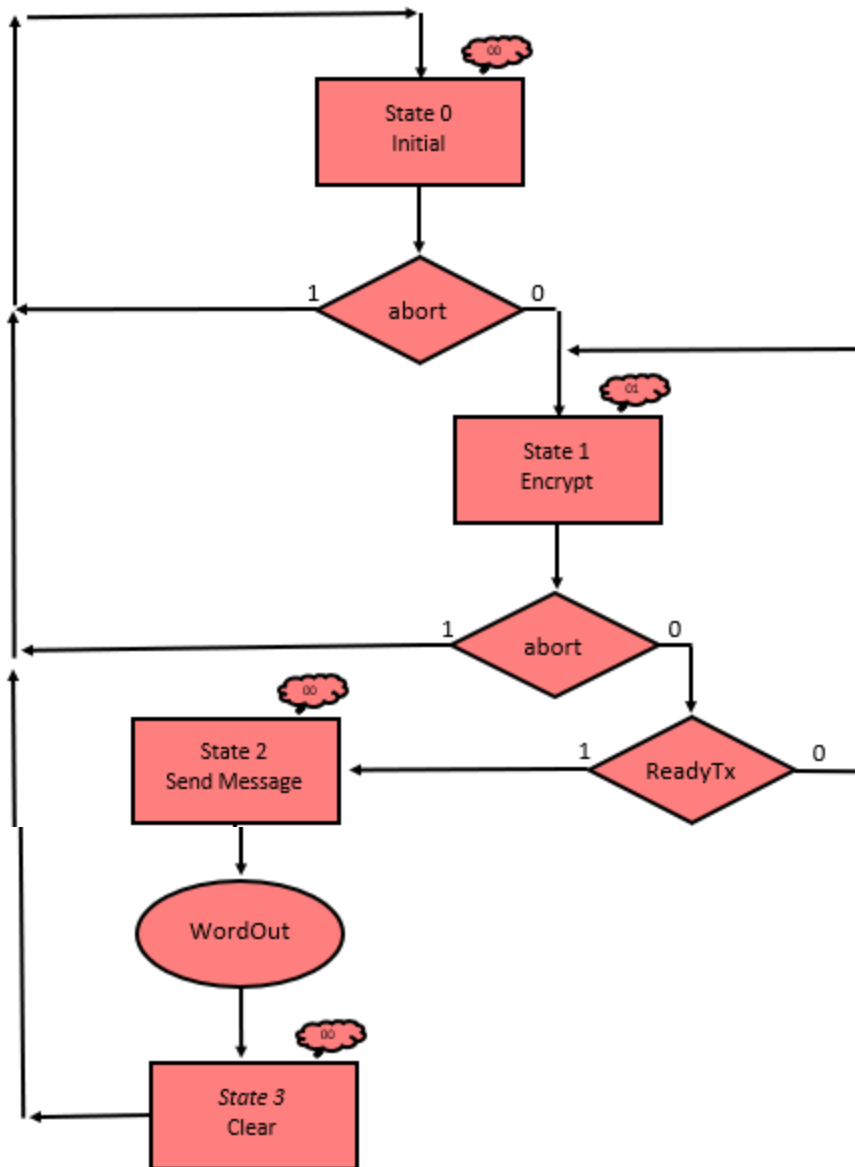


Fig (10) SM Chart Encryption Device:



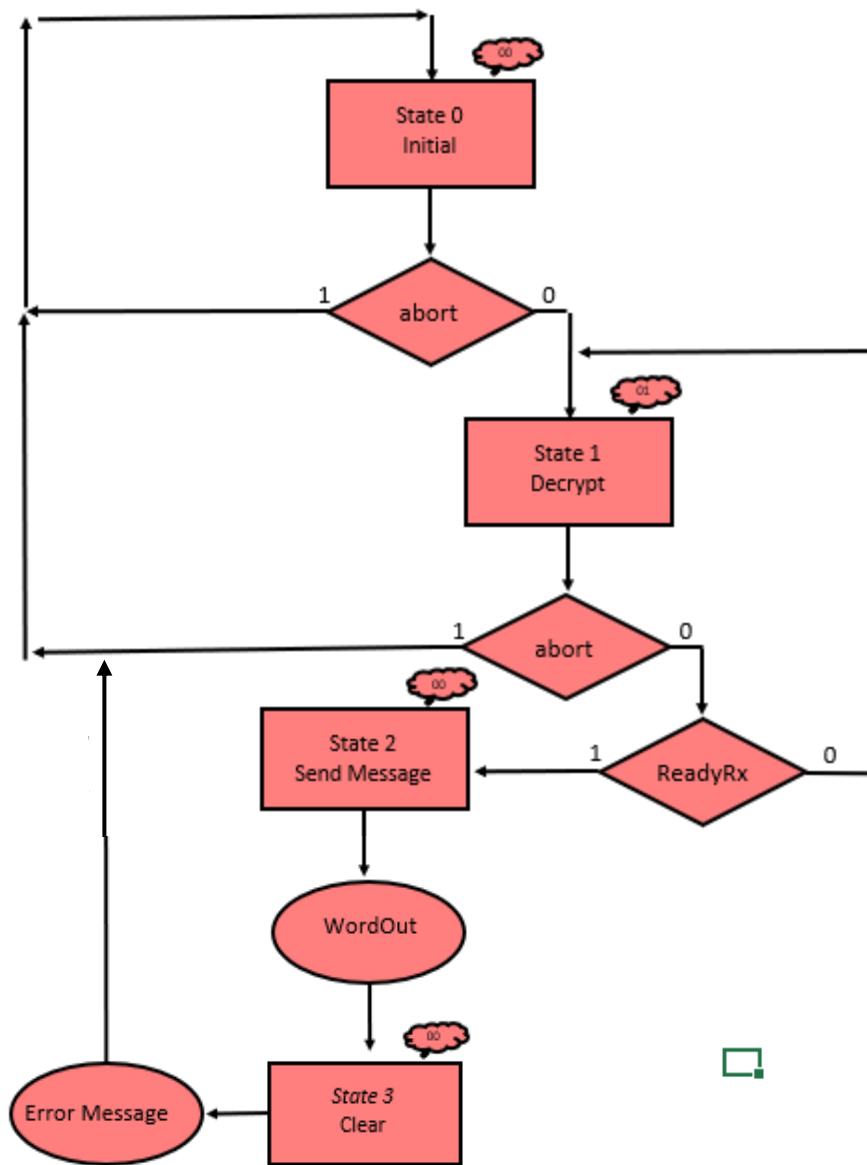


Fig (11) State graph for encryption and state table:

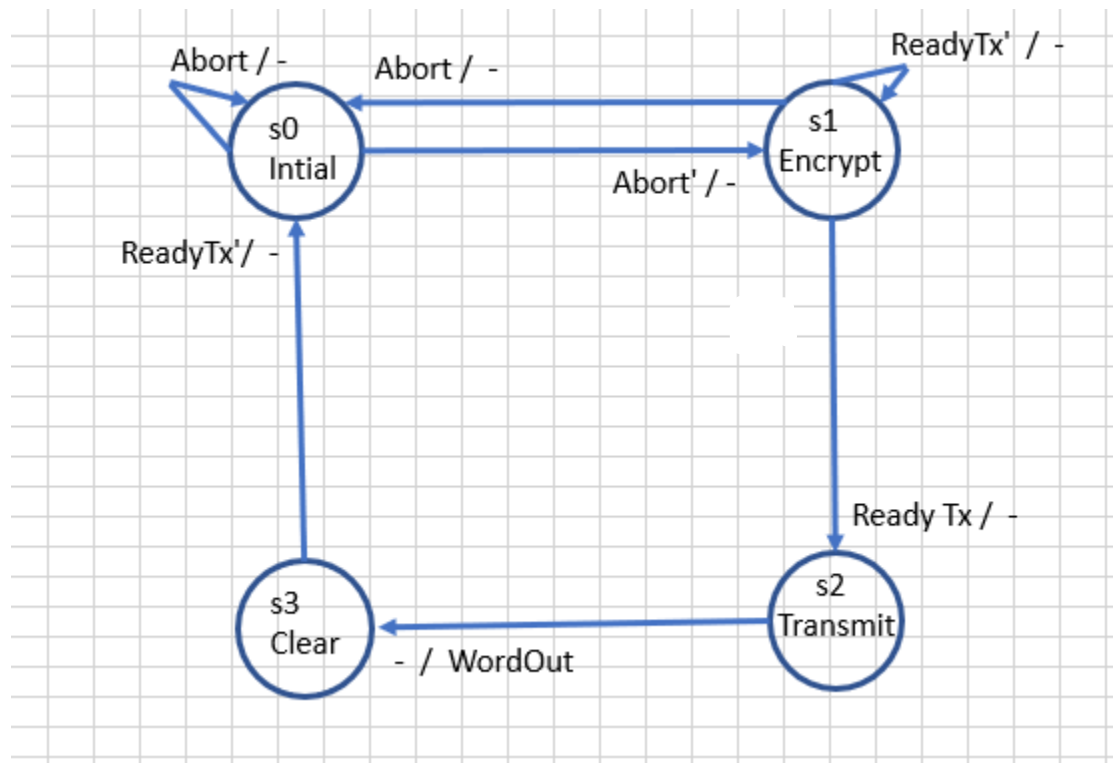

state table				
PS	NS		output	
	x=0	x=1		
s0	s1	s0	-	
s1	s1	s2	-	
s2	-	s3	WordOut	
s3	s0	-	-	

Fig (12) State Graph for Decryption and State Table:

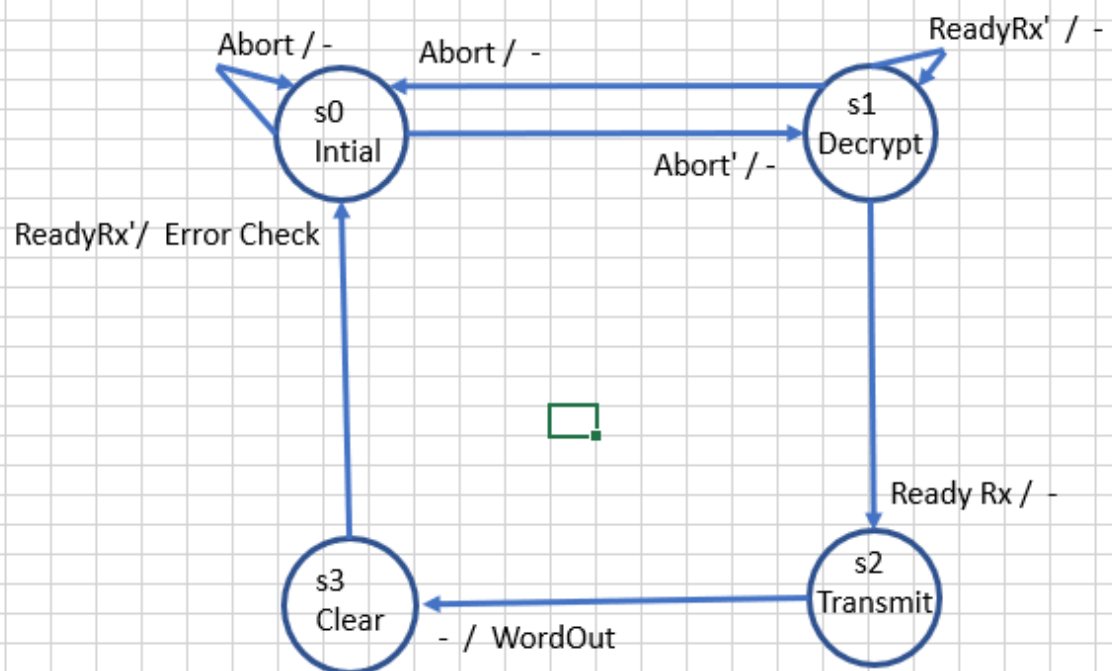

	x=0	x=1	z	
s0	s1	s0	-	
s1	s1	s2	-	
s2	s3	s3	wordOUT	
s3	s0	s0	ErrorCheck	

4. Circuit operation:

The encryption circuit is constructed by using three inputs Clock, Abort, and CharIn; as well as 2 outputs WordOut and ReadyTx. The clock input will be used to get the 16 bits that comprise the word being encrypted. Abort is a synchronous input being used as a clear when set equal to one, this will cease all operations and reset the circuit to state 0. CharIn is made into a 16-bit array used to store the 16-bit ASCII character with only 7 bits being used. We have WordOut set as a 16-bit array to output the now encrypted ASCII character. The output ReadyTx is being used and initially set to 0 as a controller to tell the circuit when to transmit by changing from 0 to 1. Four states are being used in order to realize the encryption function. When abort is set to 1 or the functions begins state 0; this will set the output to 0 to initialize, and ReadyTx is set to 0 to stop loading; If abort is set to 0 then state 1 can begin. State 1 is being used to encrypt an ASCII character using $\text{WordOut} = \text{CharIn} + 16'b1000011110100101$. The counter is increased in state one to read the next variable assigned; this will sequentially continue to read each word until all 200 words are read. Once all 200 words are read the function moves onto the third state, state 2, here the function will transmit the encrypted message to the decryption device. Once state two has been completed the fourth and final state, state 3, in this state the machine will clear the transmit buffer clear the input buffer and reset back to state 0.

The decryption circuit works similar to the encryption circuit using three inputs clock abort CharIn; as well as two outputs WordOut and ReadyRx. These I/O's work in similar fashion the difference being this device serves to decrypt. The clock input will be used to get the 16 bits that comprise the word being decrypted. CharIn is made into a 16-

bit array used to store the 16-bit ASCII the additional nine bits are now being used for the encryption. The output ReadyRx is still being used and initially set to 0 as a controller to tell the circuit when to transmit by changing from 0 to 1. Four states are being used in order to realize the decryption function. When abort is set to 1 or the functions begin state 0; this will set the output to 0 to initialize, and ReadyRx is set to 0 to stop loading; If abort is set to 0 then state 1 can begin. State 1 is being used to encrypt an ASCII character using $\text{WordOut} = \text{CharIn} - 16'b1000011110100101$. The counter is increased in state one to read the next variable assigned; this will sequentially continue to read each word until all 200 words are read. Once all 200 words are read the function moves onto the third state, state 2, here the function will output the message. Once state two has been completed the fourth and final state, state 3, in this state the machine will clear the transmit buffer clear the input buffer and reset back to state 0. The encryption device will output another result with the original text to verify output.

5.Simulation Results with annotation:

Fig (5) encryption input (raw):

TIME(ns)	index	value(encrypted)
tranmission to follow:		
30	1	1000011111101110
50	2	1000011111000101
70	3	1000100000001101
90	4	1000100000000110
110	5	1000100000011011
130	6	1000100000001010
150	7	1000011111000101
170	8	1000011111011000
190	9	1000011111000101

Fig (6) encryption output(encrypted):

3850	192	1000011111000101
3870	193	1000011111110001
3890	194	1000011111111010
3910	195	1000011111101000
3930	196	1000011111110000
3950	197	1000011110100101
3970	198	1000011110100101
3990	199	1000011110100101
4010	200	1000011110100101
{ reset, ready for next TX }		
tranmission to follow:		

Fig(7) decryption input is same as encryption output:

3850	192	1000011111000101
3870	193	1000011111110001
3890	194	1000011111111010
3910	195	1000011111101000
3930	196	1000011111110000
3950	197	1000011110100101
3970	198	1000011110100101
3990	199	1000011110100101
4010	200	1000011110100101

{ reset, ready for next TX }

transmission to follow:

Fig (8) decryptor output with verification

message to follow:

I have 3 tons of gold that I need you to pick up.
 Be at Melli Bank 35.686 51.393 no later than 202005271300Z.
 Bring an airplane, some tools, and 5lbs of potatoes.
 Pay Dr. Greg when done.
 GOOD LUCK

{ reset, ready to decrypt next RX }

SECOND TRANSMISSION, MAKE SURE IT SAME AS FIRST :

I have 3 tons of gold that I need you to pick up.
 Be at Melli Bank 35.686 51.393 no later than 202005271300Z.
 Bring an airplane, some tools, and 5lbs of potatoes.
 Pay Dr. Greg when done.
 GOOD LUCK

message to follow:

6.Encountered Problems and how they were solved:

ASCII input and output are hard to realize and very tedious to obtain manually.

To overcome this obstacle and not have to manually code thousands of entries, we used simple programs to generate the segments of code that we needed. The computer program also helped guide the design, get a working model rapidly, and verify circuit output.

Working from home proved difficult when attempting to realize a full hardware implementation so this code is done with only the software in mind and written behaviorally vs structurally.

7.Any information regarding the project that might be interesting:

The code used to encrypt the algorithm is done by adding +1957 in binary to the binary ascii value. 1957 was chosen because it is the year UNLV was founded. This project was done in self-isolation. This project was done during self-isolation and was done through video messaging, Google Drive, and EDAplayground. As lab partners throughout the semester, we completed all 12 labs together. The first few labs were very basic, and we did not know much about sequential circuits. The basics are important in logic design; every topic is interrelated and adds a new level of abstraction to build upon in a later lab. Circuitry has to be properly arranged to function as desired.

It is notable that the designer needs to have the skills with both combinational and sequential circuits. With this project, we were able to apply the majority of principles that we learned throughout the semester. Working with encryption forced us to handle much larger data sets, but we found that if you can handle 2 in a row, then 200 is the same thing. The encryption scheme is very weak for simplicity, and because we are short on time and quarantined can be anything you want as long as there is an algorithm or look up table to decrypt. If decryption can't be done, then it defeats the purpose. If someone can decrypt the message, then that also defeats the purpose. But this scheme can be expanded or modified in any way. This started to get very involved as soon as work began.

8. Conclusions:

In conclusion there are some big numbers to work with and we Implemented a circuit without any I/O or ability to demonstrate, as this was done during virus outbreak of 2020, this makes it all theoretical. C++ was a good way to get the idea in writing and provides a somewhat easy transition into Verilog code. At least you can use some of the existing functions to generate some of the 1000's of inputs you will need. The array index of C++ being reversed.

To realize these functions Verilog was used to code both the encryption and decryption devices. Two test benches are written respectively for the encryption and decryption device. The test bench stimulates this circuit by acting as the buffer for an arbitrary plain text input stream. Both devices Input 200 words of 16-bit length and then

output 200 words of 16-bit length. If the message is less than 200 words, the NULL character will be encrypted. This project is comprised of 5 program files: one for getting the ascii message, a function for encryption, its respective testbench function, a decryption function, and its respective testbench.

9. Program Files:

The c++:

<https://repl.it/@davenakasone/20200424-lab12-v2>

The proof of input:

https://www.edaplayground.com/x/52_8

The encryptor:

<https://www.edaplayground.com/x/3hWW>

The decryptor:

<https://www.edaplayground.com/x/2j7c>

Google Drive:

<https://drive.google.com/open?id=1hB0f9nqWGWZmv1ZEqQpXNPdQT1TQsS0r>